 


Metastability & Clock Domain Crossing Techniques

Gabriel Cojocaru


Review of Flip Flop Setup and Hold Time

- Considering D-type edge-triggered flip flops
- Just before and just after the clock edge, there is a critical time region where the D input must not change
- The region just before the clock edge is called **setup time** (t_{su})
- The region just after the clock edge is called **hold time** (t_h)
- Every FF has minimum required values for t_{su} and t_h




Review of Flip Flop Setup and Hold Time

 - Synchronous circuit minimum cycle time is effected by setup time
- Between clock edges, the path between two FFs is composed of
 - clock to Q delay of FF0 (t_{ckq})
 - propagation delay through combo logic (t_{pd})
 - the required setup time (t_{su}) of FF1




Review of Flip Flop Setup and Hold Time

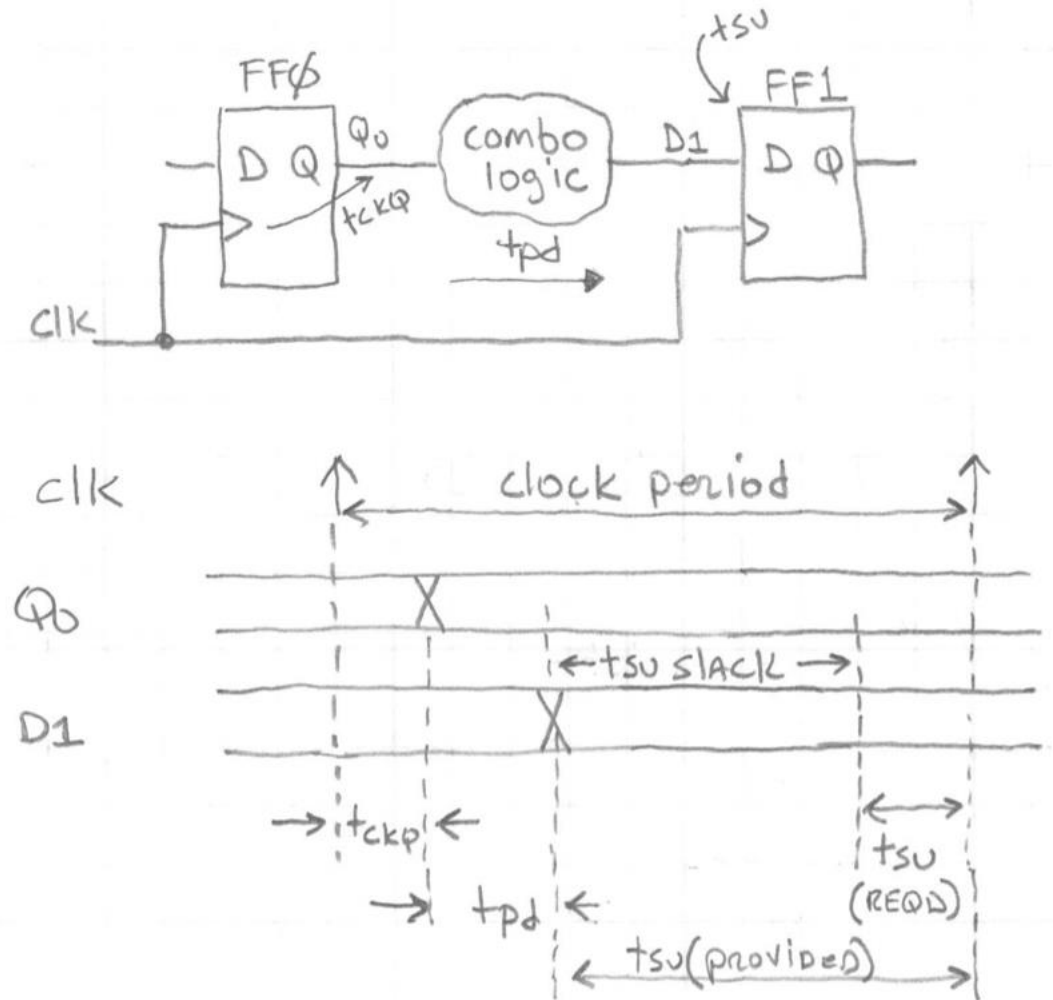- The circuit provides setup time as a function of the clock period T_{ckq} , and the combinatorial logic delay T_{pd}
- The flip flop requires a certain T_{su} to operate correctly
- The difference between the provided setup time and the required setup time is called **setup time slack**
 - Positive slack is good



Review of Flip Flop Setup and Hold Time

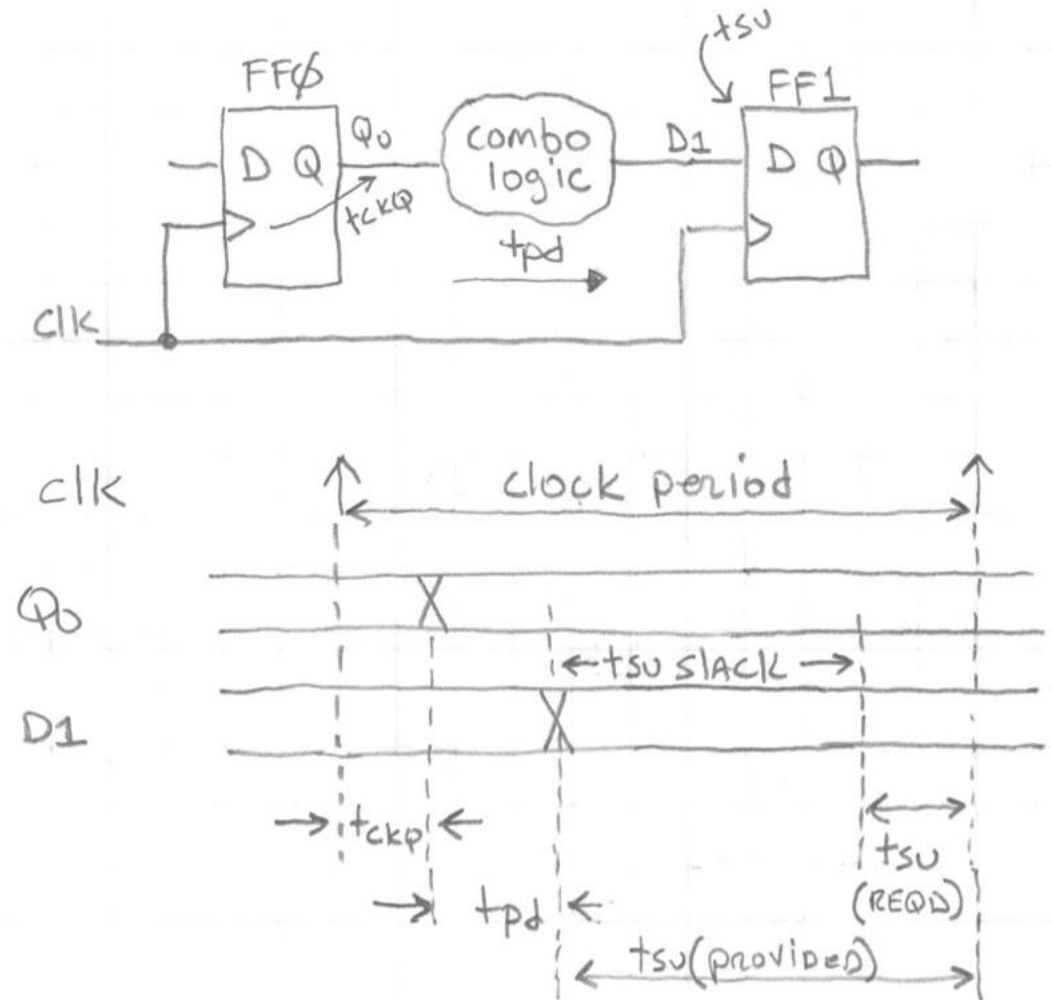- In the same fashion, the flip flop requires the data at the D input be stable for a certain T_h period after the clock edge to operate correctly
- The hold time is a function of the T_{ckq} + T_{pd} (clock-to-Q and propagation delay)
- Hold time slack is the difference between the provided hold time and the required hold time




Metastability

- In modern ICs, data is often shared between IPs and functional blocks operating at different clock frequencies
- Many synchronous systems need to interface with asynchronous data sources
 - Interrupts from peripherals (I/O devices, key strokes, etc.)
 - Data transfers with different clock rates (PCIe, Ethernet, etc.)
 - Often these data sources have no known timing relationship to the cpu/system clock
- If not properly addressed, can cost the company a lot of money and someone their job!
- It is something that is often brought up in interviews


Metastability

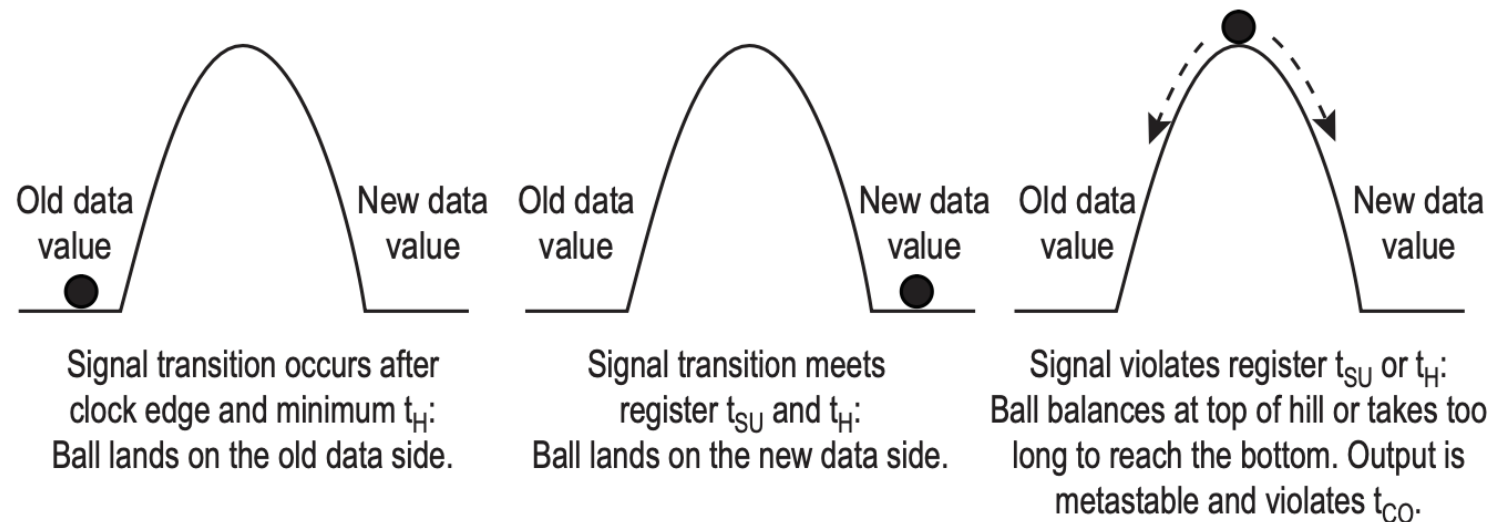- Refers to signals that aren't a stable 0 or 1 for a some period of time during normal operation
- Cannot be avoided, but the detrimental effects can be neutralized




Metastability

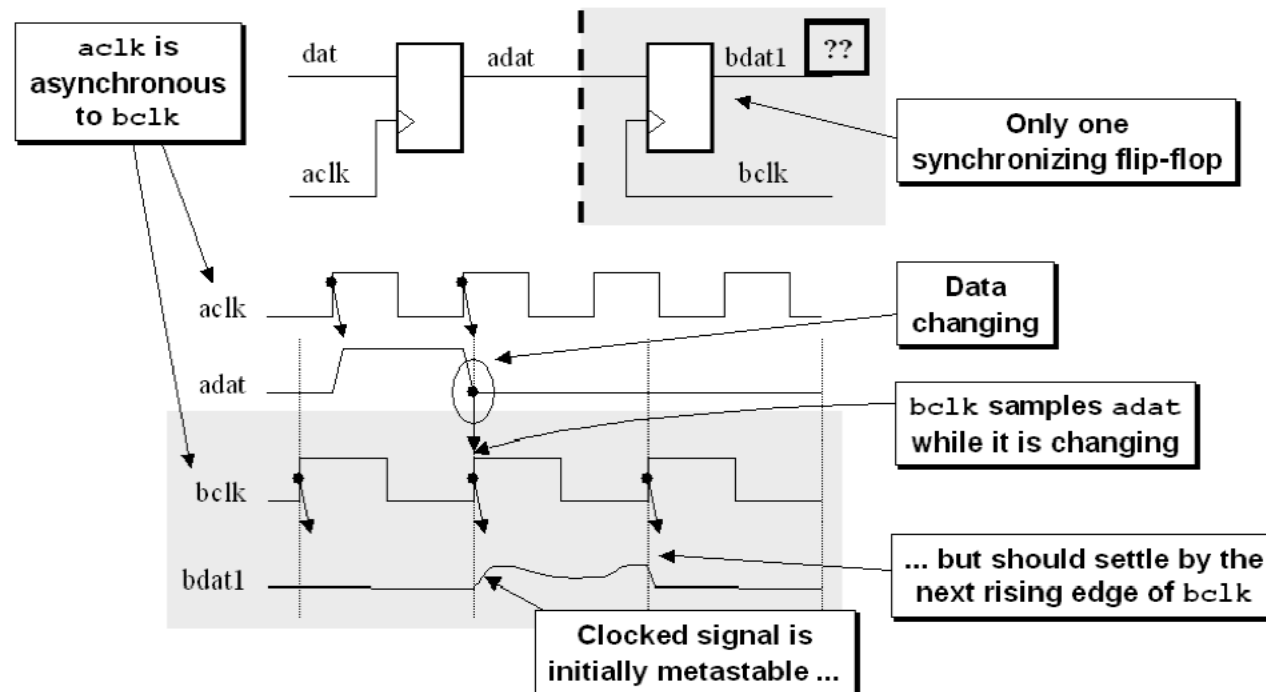- Signal generated in one clock domain that is changing too close to the rising edge of a clock in another clock domain causes the output to go metastable



Metastability

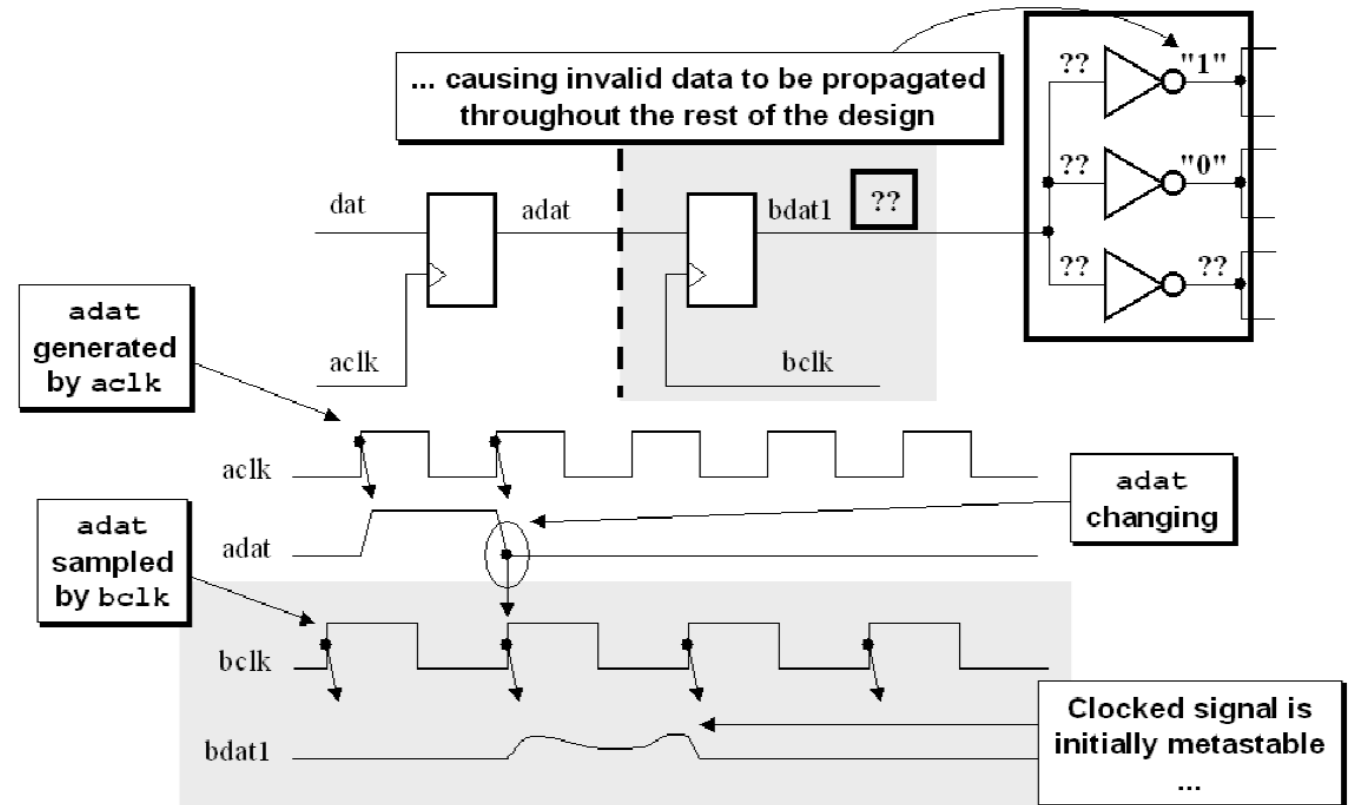- Why is it a problem?
 - Metastable outputs in the receiving clock domain can propagate to the rest of the design affecting state machines, control logic, etc.




Metastability

- How do we solve this?
 - Synchronizers!
- Two scenarios
 - It is not necessary to sample every value in the receiving clock domain, but it is important that the sampled values are accurate. Ex: read and write gray code counters used in async FIFOs (which we will discuss later)
 - The signal needs to be properly acknowledged before it is allowed to change again

Two flip-flop synchronizer

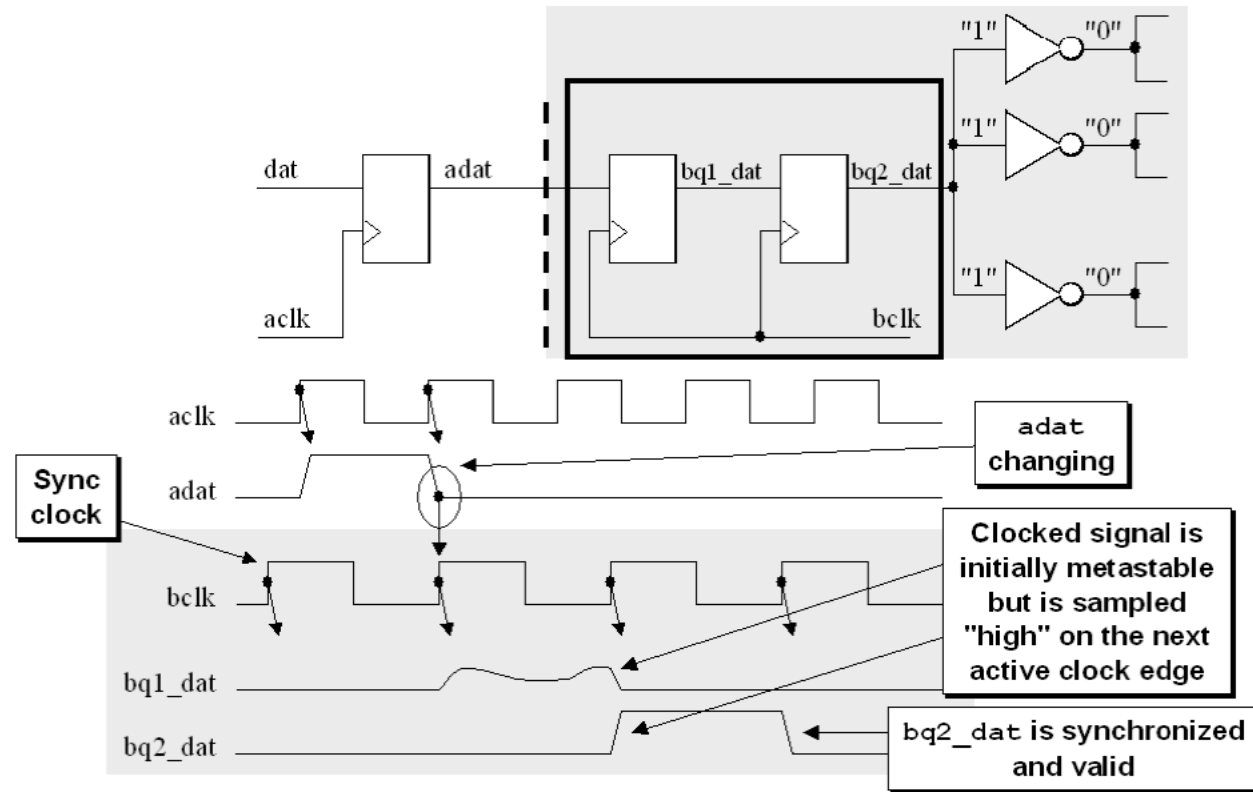- Most common synchronizer used by digital designers is a 2ff synchronizer



Two flip-flop synchronizer

- It is possible that the metastability will propagate through the second ff
- The probability of the time between synchronization failures (MTBF) is a function of multiple variables


$$MTBF = \frac{1}{f_{clk} * f_{data} * X}$$

The diagram illustrates the MTBF formula with three callout boxes. A box labeled 'Synchronizing clock frequency' has an arrow pointing to f_{clk} . A box labeled 'Data changing frequency' has an arrow pointing to f_{data} . A box labeled 'Other factors' has an arrow pointing to X .

- We can see that high speed designs are more prone to synchronization issues


Three flip-flop synchronizer

 - In very high-speed designs, MTBF of a two-flop synchronizer is too short, so a 3rd flop is added




Synchronizing Signals From Sending Clock Domain

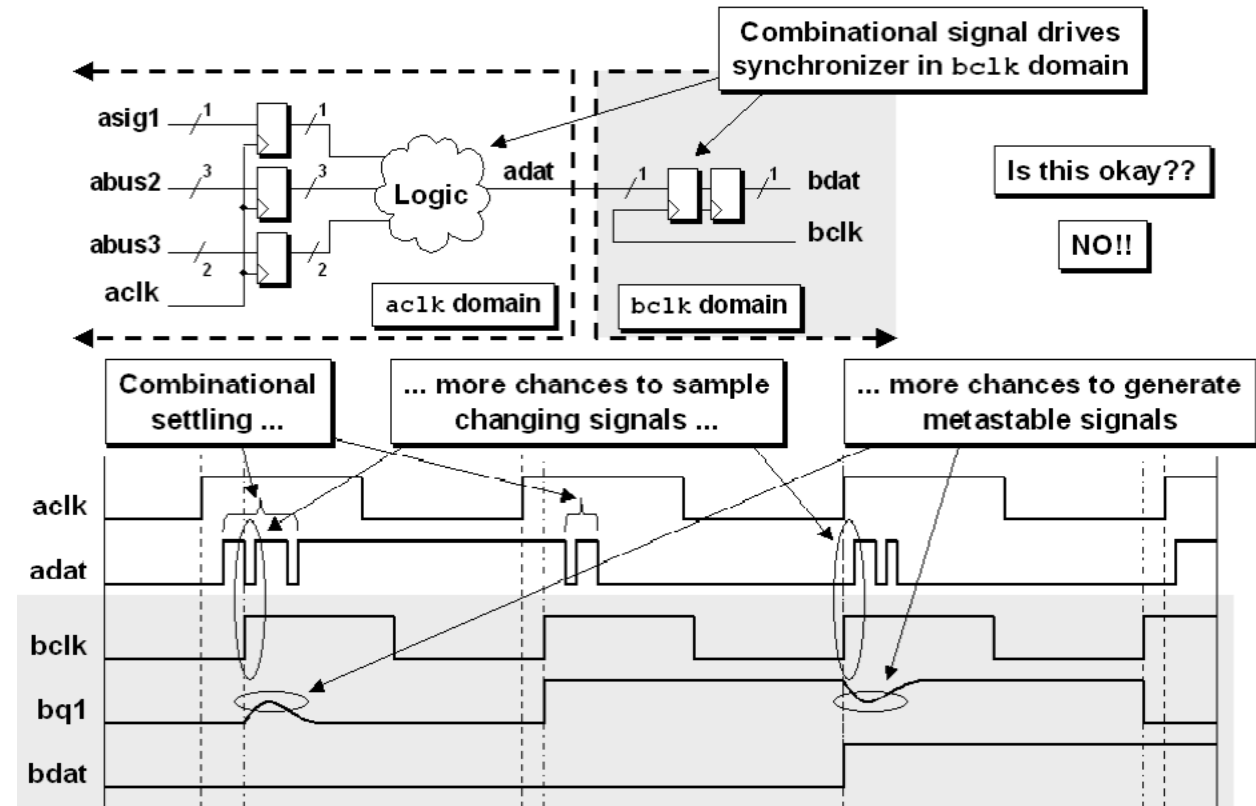- Consider a case where signals in the sending clock domain aren't registered after passing through combinatorial logic as seen below
- Combinatorial settling increases the chance of data transitions or glitches on *adat*, reducing MTBF



Synchronizing Signals From Sending Clock Domain

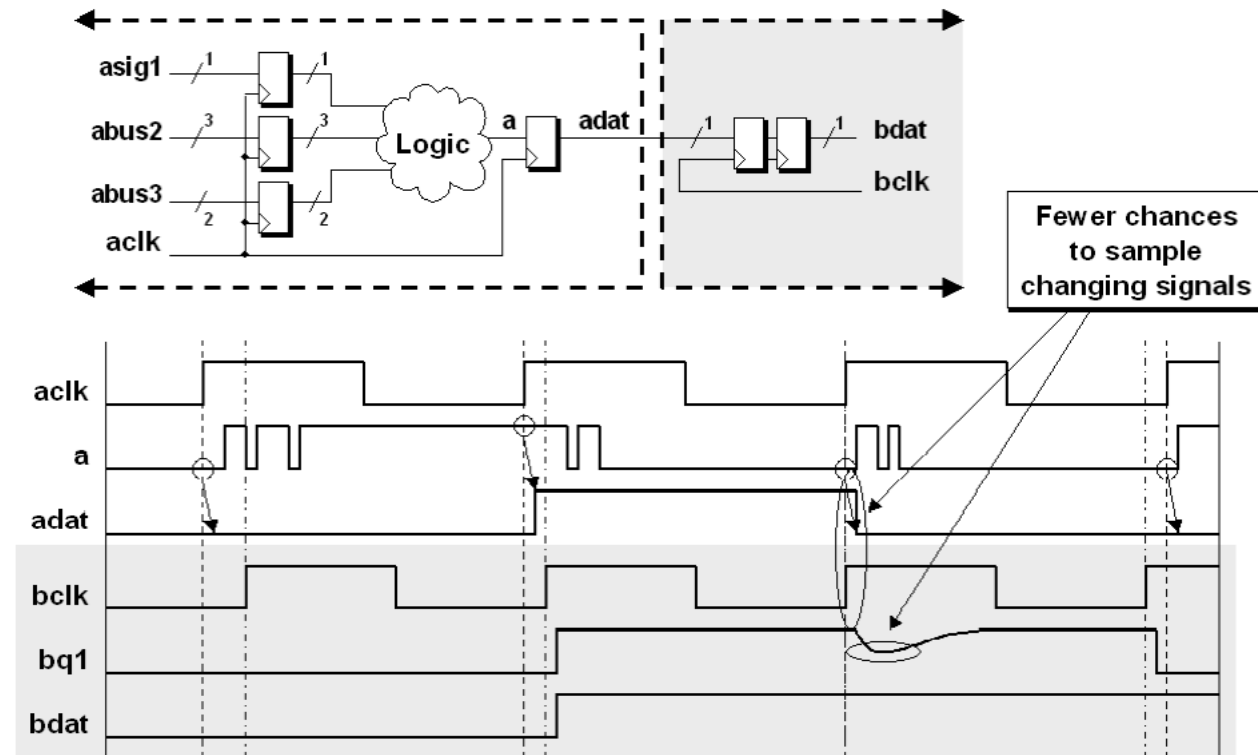- Therefore, signals that cross clock domains should first be sampled in the sending clock domain as shown here



Requirements for proper CDC


- Synchronizing slower signals into a faster clock domain is generally not an issue (at least 1.5X)
 - The signal will be sampled one or more times in the receiving clock domain
 - Two flip-flop synchronizers can be used for single bit signals
- Sampling faster signals in a slower clock domain introduces some problems

Synchronizing Fast Signals Into Slow Clock Domain

- One issue with synchronizers is the possibility that a signal in the sending clock domain changes multiple times before it can be sampled in the receiving clock domain
- When missing samples is not an option, two approaches are possible
 - Open-loop solution – capturing signals without acknowledgement
 - Closed-loop solution – passing back an ack signal into the sending clock domain


Problem 1: Fast Pulse

- The pulse can go low -> high -> low in the sending clock domain and be completely missed in the receiving clock domain

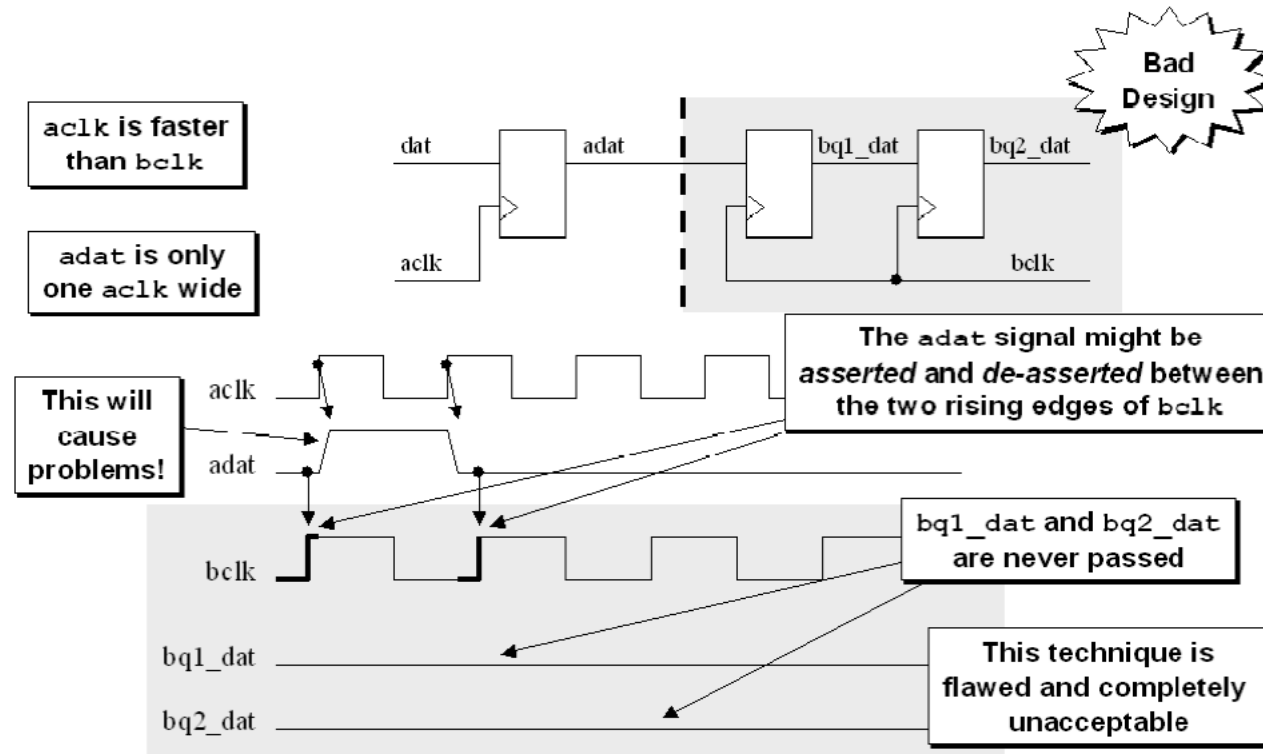

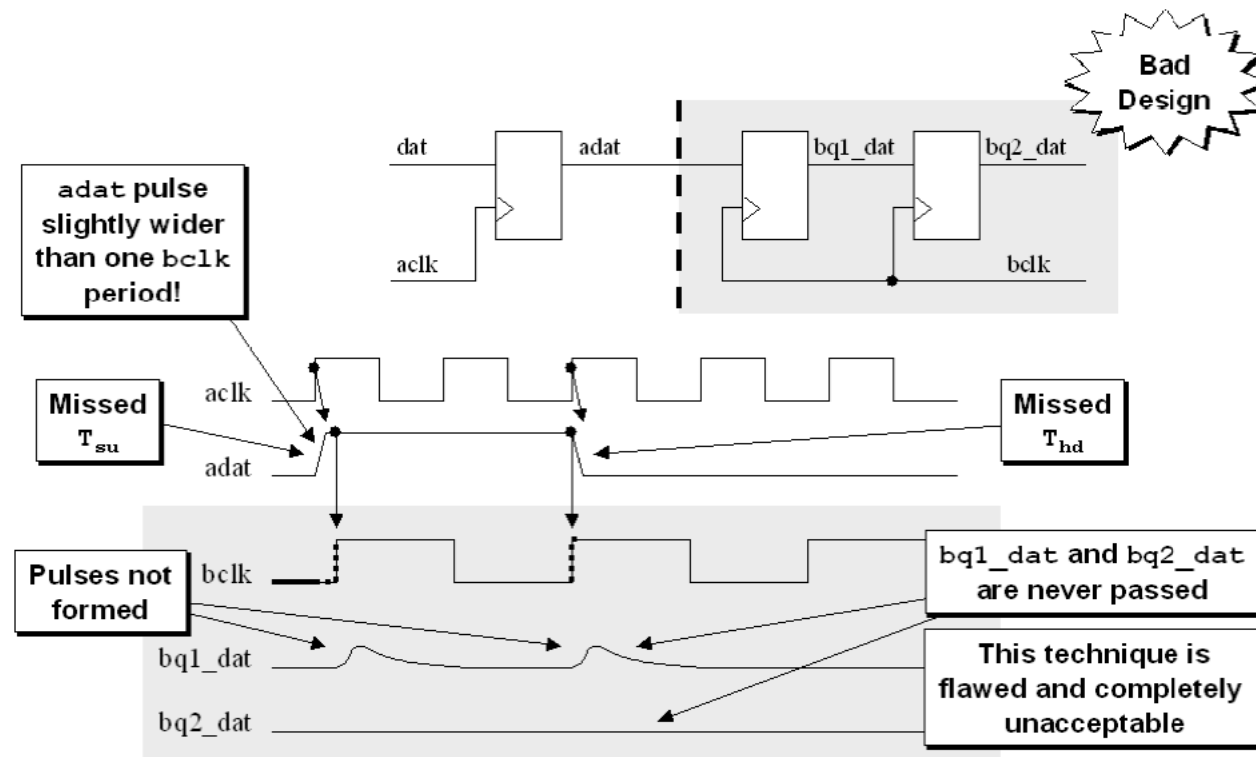
Problem 1: Long Pulse (but not long enough)

- If the pulse is slightly wider than the period of the receiving clock, although rarely, it can miss setup/hold times as shown




Open-loop solution – 2ff synchronizer

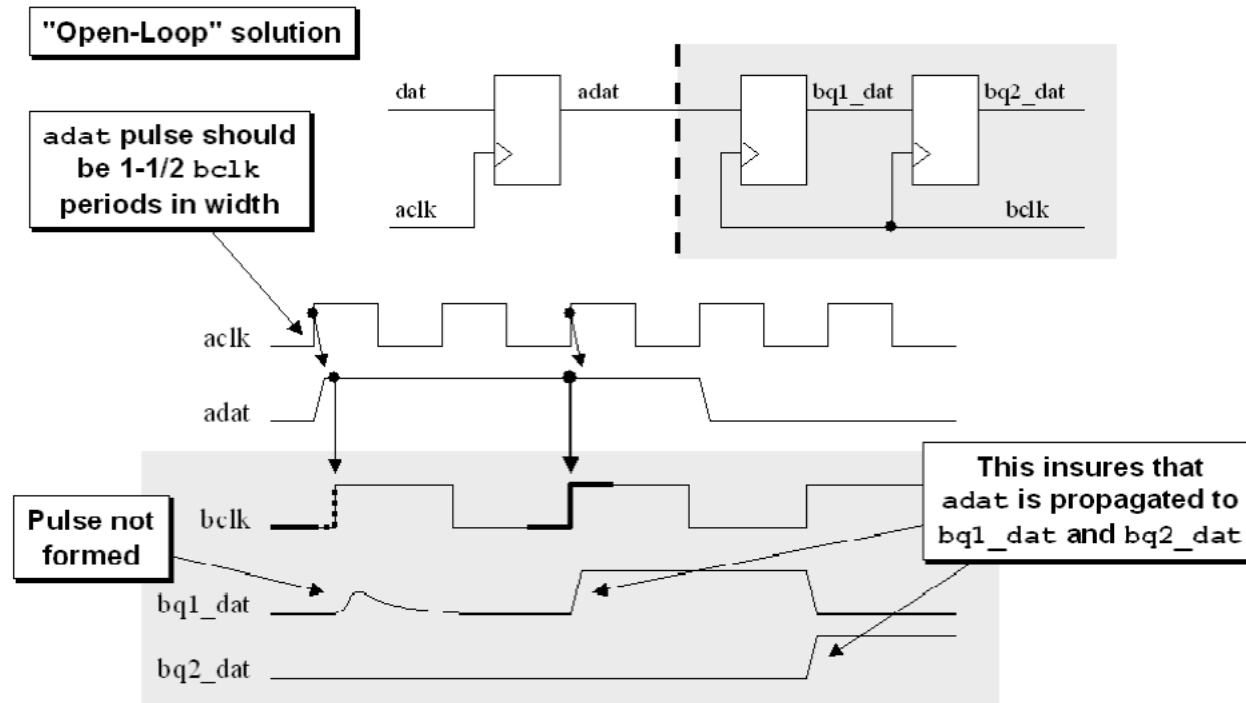- Assert the CDC signal for a period of time longer than the period of the receiving clock



Closed-loop solution

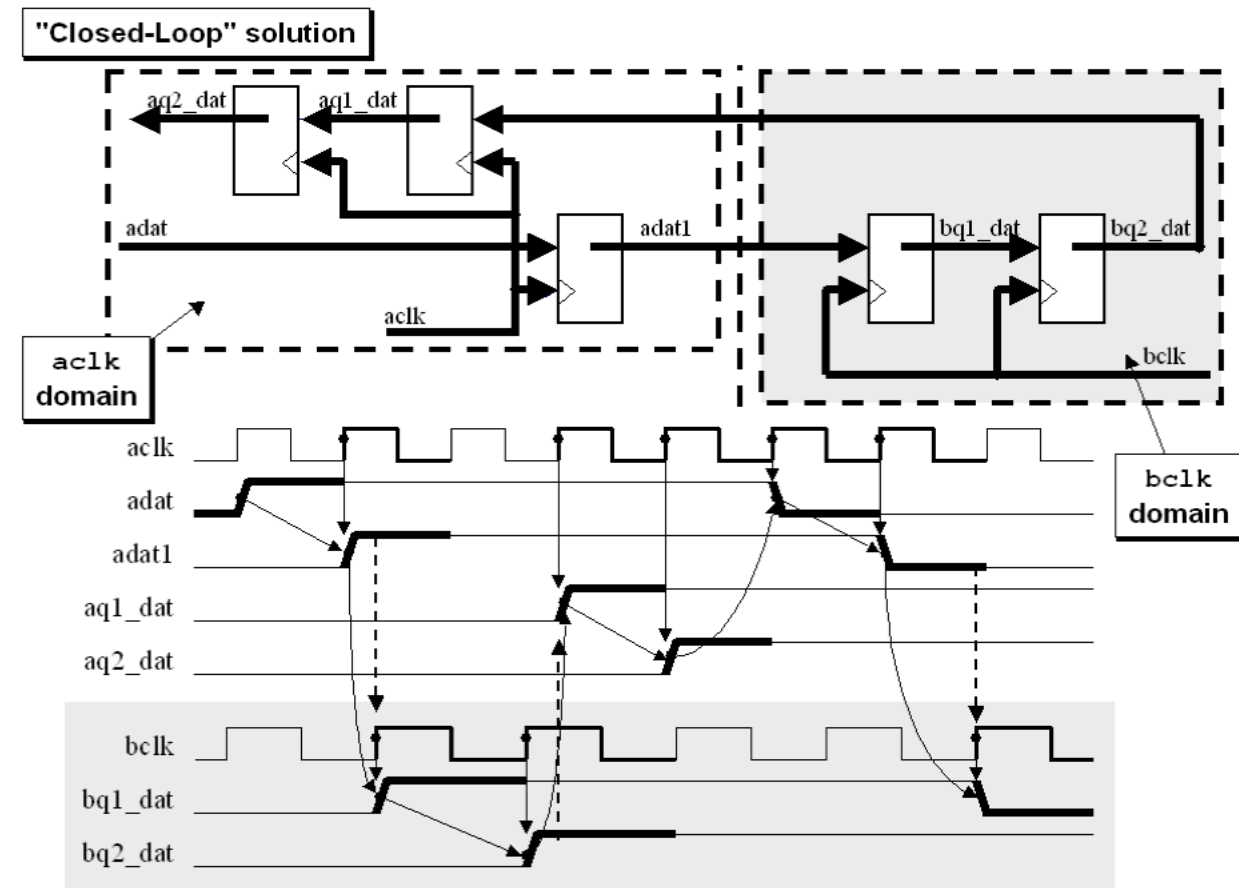- Send a synchronized acknowledgment signal
- Safe technique to ensure the control signal was sampled correctly
- Introduces delay due to the extra synchronization logic



Multi-bit Signals CDC


- Simple synchronizers do not guarantee safe data delivery
- In addition to signal synchronization, it is also important to ensure synchronized sampling of multi-bit data
- Multi-bit signals synchronized to one clock will experience data changing skews that might cause bits to be sampled on different rising edges in the new clock domain
 - Even with perfect trace length matching, difference in rise/fall times and process variations across a die introduce enough skew

Multi-bit CDC Strategies

- Multi-bit signal consolidation
 - When possible, consolidate multiple bits into one before crossing clock domains
- Multi-Cycle path formulation
 - Synchronized load signal to pass multiple unsynchronized CDC bits
- Pass multiple CDC bits using gray codes


Bit Consolidation – Potential Issue

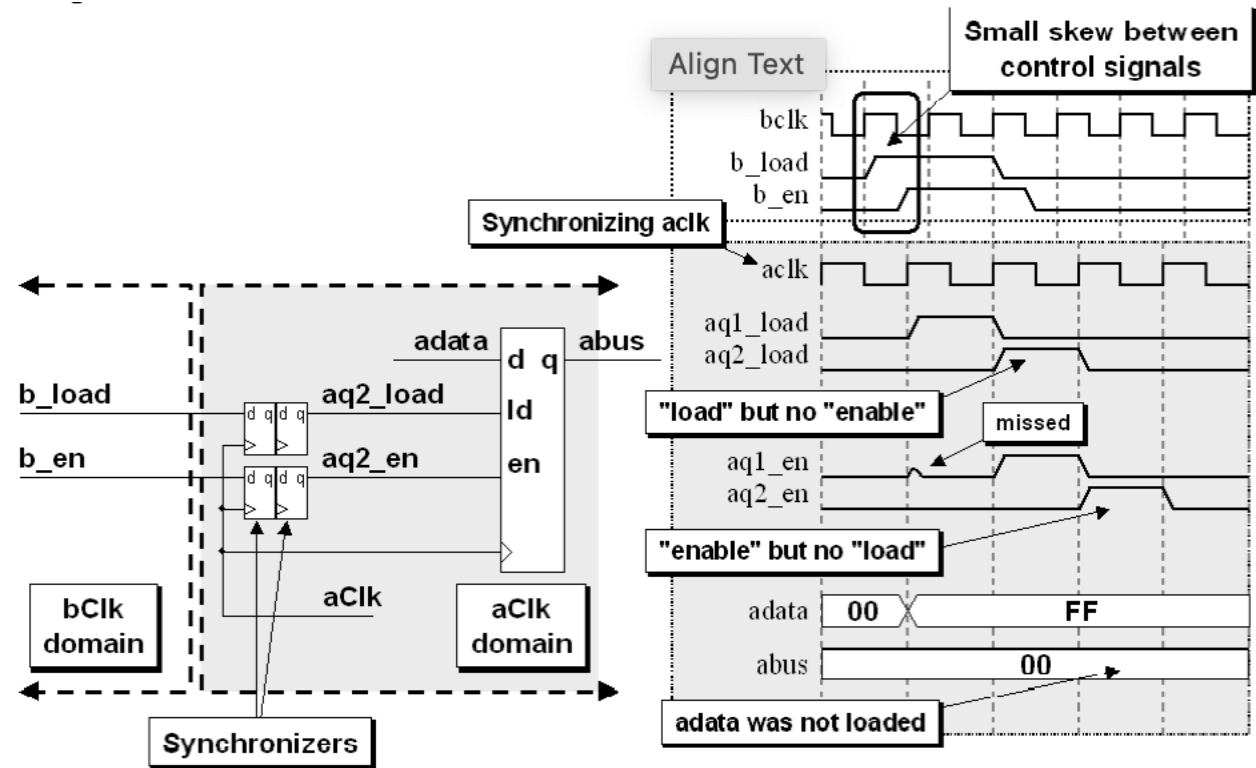- If both control signals are needed to load data value into a register, but one of them is synchronized on a different rising edge (due to skew), data would not be loaded into the register




Bit Consolidation – Solution

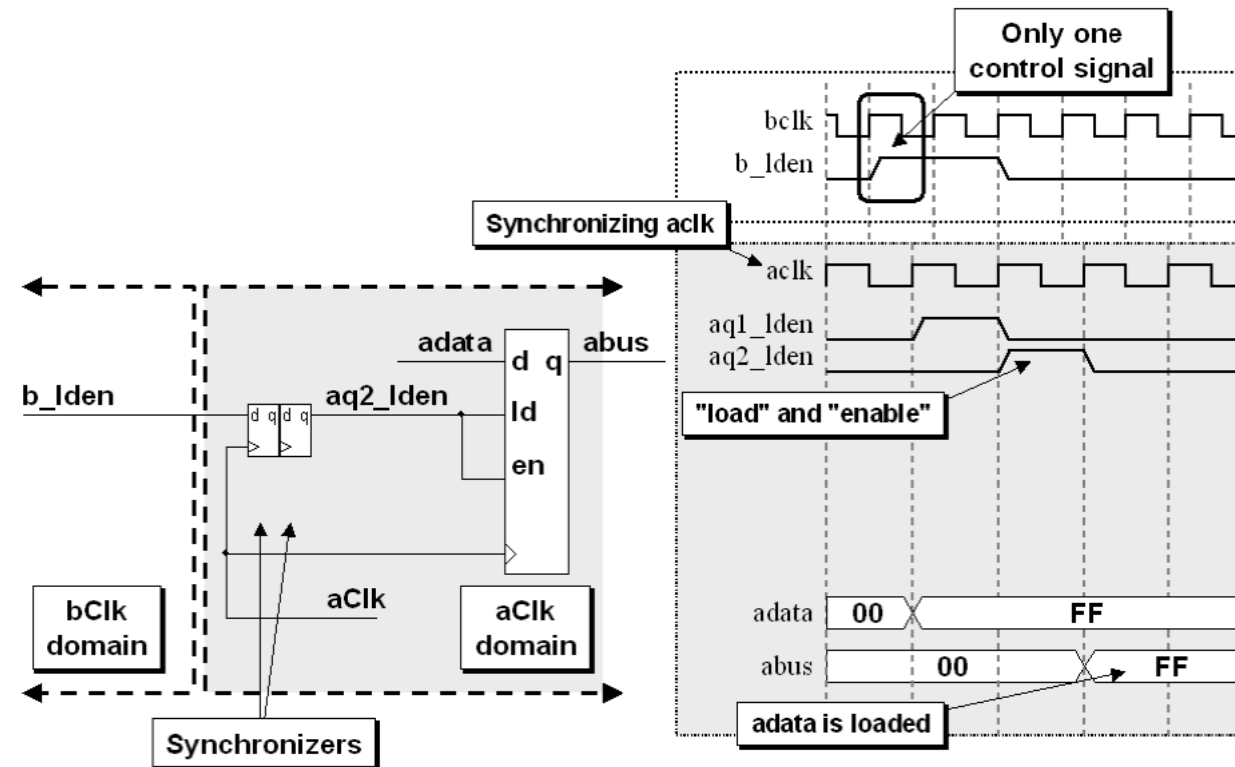- Consolidate both signals into one b_iden and synchronize it



Multi-Cycle Path Formulation

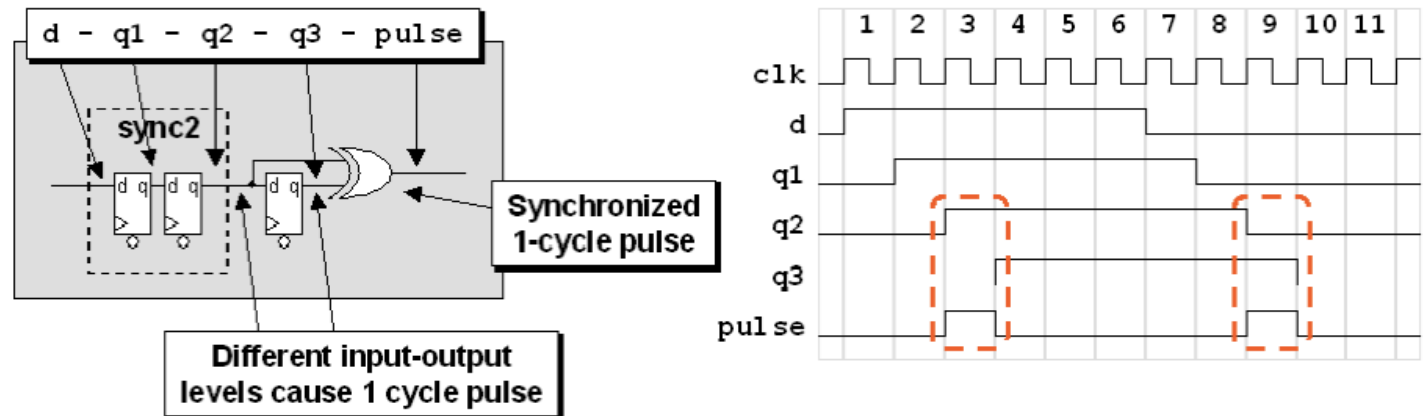- Simultaneously send unsynchronized data to a receiving clock domain, paired with a synchronized control signal
- Advantages:
 - The sending clock domain does not need to calculate the appropriate pulse width between clock domains
 - Only one control signal needs to be synchronized
- The control signal is passed through a synchronized pulse generator



Multi-bit CDC using FIFOs

- Passing multiple bits, either data or control bits, can be done using asynchronous FIFOs
- An Async FIFO is a shared memory or register buffer where data is inserted in the write clock domain and read in the receiving clock domain
- Most of the hard work in designing an Async FIFO is done through the synchronization of the read and write pointers


A bit on Gray Codes

- Gray code is a binary code where each successive value differs from the previous one by only one bit: 000,001,011,010...
- Eliminates the need with trying to synchronize multiple changing CDC bits
- Binary to Gray conversion can be simply be done like this:


```
assign gray = bin ^ (bin >> 1);
```

Async FIFOs

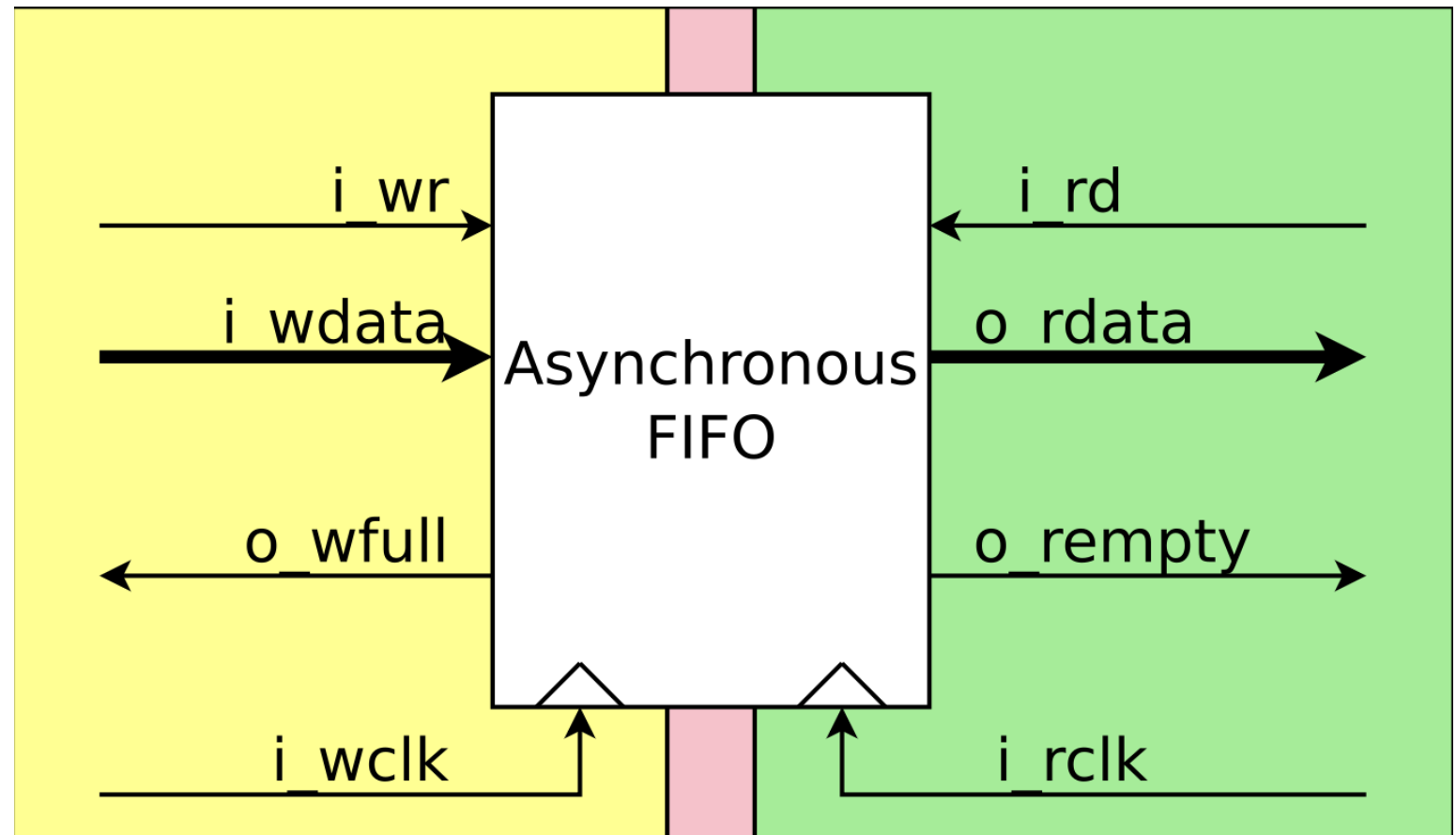- A basic async FIFO block diagram might look like this



Async FIFO – cont'd

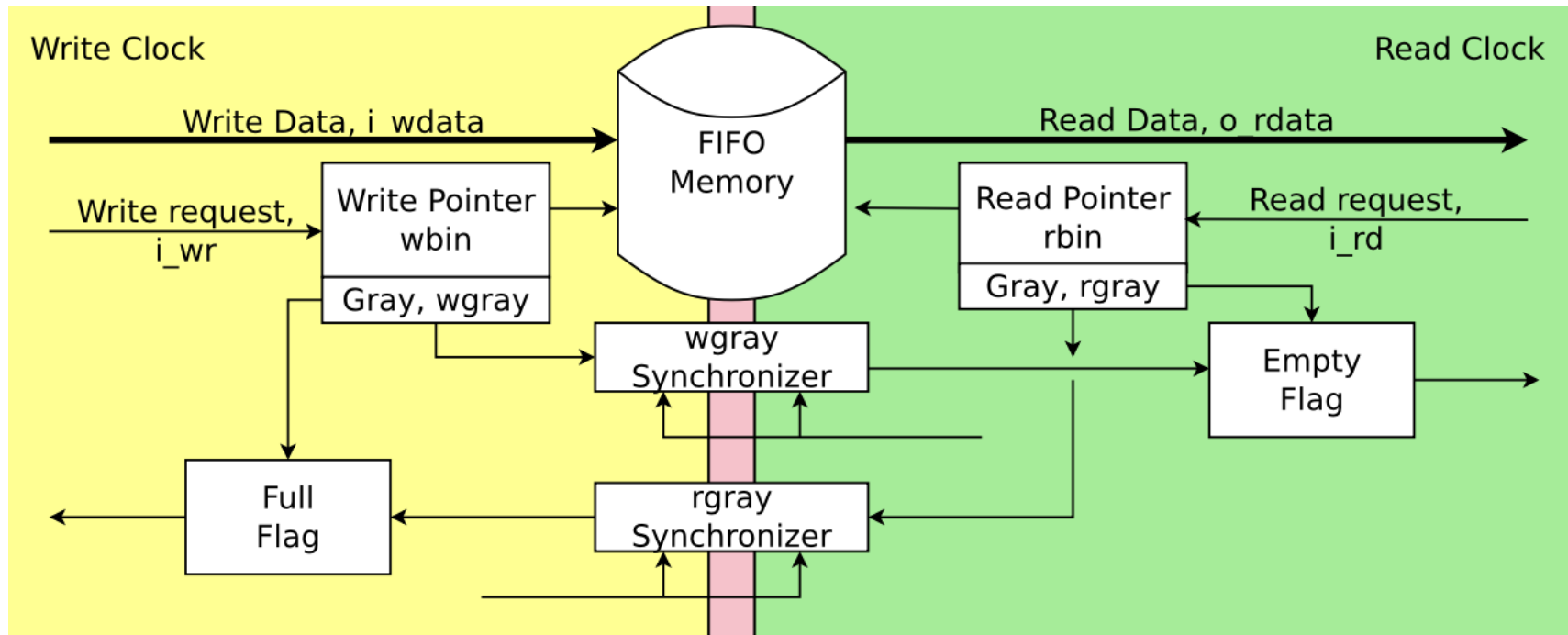

Async FIFO – cont'd

- Most work is done around generating the empty and full flags
- FIFO Full flag is set when the write pointer catches up to the synchronized read pointer (in the write clock domain)
 - Extra attention needs to be paid to the case when the write pointer wraps around one more time than the read pointer
- Empty flag is set when the read pointer is equal to the write pointer synchronized in the read clock domain
- Assignment 6 will be based on this, and we will cover Async FIFOs in more detail on Friday

Questions?

Thank you!